

WEEKLY CLASS TEST


Batch : S1

SOLUTION

Date : 13/08/2023

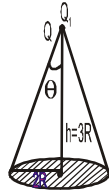1. [B] When charge is at O_1 the flux through the face having radius $2R$ is

$$w_1 = \frac{q}{v_0} \cdot \frac{2f(1 - \cos \theta)}{4f}$$



$$= \frac{q}{v_0} \cdot (1 - \cos \theta)$$

$$= \frac{q}{2v_0} \left[1 - \frac{3R}{\sqrt{(2R)^2 + (3R)^2}} \right] = \frac{q}{2v_0} \left[1 - \frac{3}{\sqrt{13}} \right]$$

Similarly,

$$w_2 = \frac{q}{2v_0} \left[1 - \frac{3R}{\sqrt{R^2 + (3R)^2}} \right] = \frac{q}{2v_0} \left[1 - \frac{3}{10} \right]$$

$$\frac{w_1}{w_2} = \left(\frac{\sqrt{13} - 3}{\sqrt{10} - 3} \right) \cdot \sqrt{10}$$

2. [C] There are two capacitor in series. Equivalent capacitance is

$$C_0 = \frac{1}{2} \left(\frac{v_0 A / 2}{d} \right) = \frac{v_0 A}{4d}$$

\therefore Charge supplied by the cell

$$Q = C_0 V = \frac{v_0 A}{4d} V$$


$$\therefore W_{batt} = QV = C_0 V^2 = \frac{v_0 A}{4d} V^2$$

3. [A] There are five capacitor each of capacitance

$$C = \frac{v_0 A}{d}$$

The arrangement is a Wheastone bridge as shown in figure.

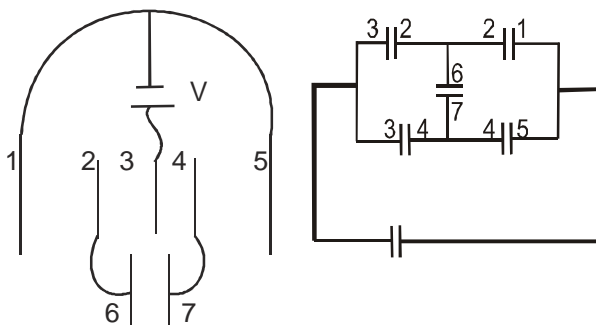It is a balanced bridge and equivalent capacitance is



$$C_0 = C = \frac{v_0 A}{d}$$

$$\therefore Q = C_0 V = \frac{v_0 A}{d} V$$

4. [B] As, $X > Y$ and $P = Q$

\therefore Potential of point a is less than of b. Current flows from b to a.

5. [B] At null deflection position, equivalent emf of cell combination (of 2 cells in parallel) is balanced against potential drop of AN length of potentiometer wire.

Now, equivalent emf of combination is

$$E_{ed} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2} = \frac{2 \times 6 + 4 \times 2}{2 + 6} = \frac{12 + 8}{8}$$

$$\therefore E_{eq} = \frac{20}{8} = 2.5V$$

and potential drop across AN length = potential drop per unit length \times length AN

Now, current in potentiometer wire

$$= I_{AB} = \frac{E}{R_{total}} = \frac{12}{4 + 4} = \frac{12}{8} A = 1.5A$$

So, V_{AB} = potential drop across AB length of wire

$$= I_{AB} R_{AB} = 1.5 \times 4 = 6V$$

Hence, potential drop across AN length


$$= \frac{V_{AB}}{I_{AB}} \times AN = \frac{6}{4} \times AN$$

$$\text{So, } \frac{6}{4} AN = E_{eq}$$

As, N is null deflection point

$$\Rightarrow \frac{6}{4} \times AN = 2.5 \Rightarrow AN = \frac{2.5 \times 4}{6} = \frac{5}{3} m$$

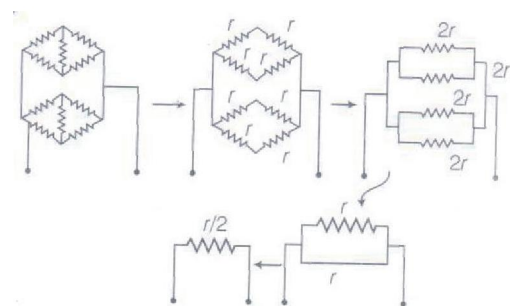6. [D] Given network of resistance is equivalent to two balanced Wheatstone bridge



As, meter bridge is balanced,

$$\therefore \frac{10}{30} = \frac{r/2}{60} \Rightarrow \frac{10 \times 60}{30} \times 2 = r$$

or $r = 40\Omega$


7. [D] At 20 cm mark, reading of voltmeter is zero
At some distance x from centre,

$$V_P = 4 \left(\frac{20+x}{40} \right)$$

and $V_Q = 2V$

$$\therefore V_P - V_Q = \frac{x}{10} \text{ volt}$$
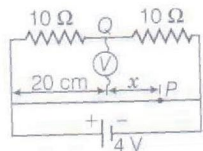
$$\Rightarrow 2 \sin f t = \frac{x}{10}$$



As, $x = 20 \sin f t$

$$\therefore \frac{dx}{dt} = \text{velocity}$$

$$= 20 f \cos f t \text{ cm/s}$$

8. [A] Ohm's law $V = IR \Rightarrow V \propto I$ (for ammeter)

$$\therefore \frac{V_2}{V_1} = \frac{I_2}{I_1} = 2$$

$$\Rightarrow 10 = 2 \times 10 \times \frac{R}{2+R}$$

$$\Rightarrow R = 2\Omega$$

9. [ABC] The force F experience by the electron (towards the +ve plate) is given by

$$F = qE = 1.6 \times 10^{-19} \times 3000 = 4.8 \times 10^{-16} \text{ N}$$

Hence the acceleration experienced by the electron [is given by

$$a = \frac{F}{m} = \frac{4.8 \times 10^{-16} \text{ N}}{9.1 \times 10^{-31} \text{ kg}} = 5.3 \times 10^{14} \text{ m/s}^2$$

Now the electron is released from the negative plate and is travelling to the positive plate. We have

$$\hat{v}_0 = 0 \quad x = 0.15 \text{ m}$$

and $a = 5.3 \times 10^{14} \text{ m/s}^2$

Substituting these values in the relation

$$x = \hat{v}_0 t + \frac{1}{2} a t^2$$

$$t = \sqrt{\frac{2x}{a}} = \sqrt{\frac{2 \times 0.15 \text{ m}}{5.3 \times 10^{14} \text{ m/s}^2}}$$

$$= 2.4 \times 10^{-8} \text{ s}$$

$$\hat{v} = \hat{v}_0 + at$$

$$= 0 + (5.3 \times 10^{14} \text{ m/s}^2)(2.4 \times 10^{-8} \text{ s})$$

$$= 1.30 \times 10^7 \text{ m/s}$$

10. [AC] Since all the changes are placed along the x -axis, the field due to all are all along the x -axis. The magnitude of total field at $x = 0$ is there-

fore just the sum of the magnitude of the field due to the individual charges.

The total field at $x = 0$ is, therefore,

$$E = \frac{1}{4\pi\epsilon_0} a \left[\frac{q}{1^2} + \frac{q}{2^2} + \frac{q}{4^2} + \frac{q}{8^2} + \dots \infty \right]$$

$$= \frac{q}{4\pi\epsilon_0} \left[\frac{1}{1} + \frac{1}{4} + \frac{1}{16} + \frac{1}{64} \dots \infty \right]$$

$$= \frac{q}{4\pi\epsilon_0} \frac{1}{1-1/4}$$

$$= \frac{1}{4\pi\epsilon_0} \left(\frac{4}{3} q \right)$$


When the consecutive charges are of opposite sign, the resultant field is given by

$$E = \frac{1}{4\pi\epsilon_0} \left[\frac{q}{1^2} - \frac{q}{2^2} + \frac{q}{4^2} - \frac{q}{8^2} + \dots \infty \right]$$



$$= \frac{q}{4\pi\epsilon_0} \left[\left\{ \frac{1}{1^2} + \frac{1}{4^2} + \frac{1}{16^2} + \dots \infty \right\} - \left\{ \frac{1}{2^2} + \frac{1}{8^2} + \frac{1}{32^2} + \dots \right\} \right]$$

$$= \frac{q}{4\pi\epsilon_0} \left[\left(\frac{1}{1-1/16} \right) - \left(\frac{1/4}{1-1/16} \right) \right]$$
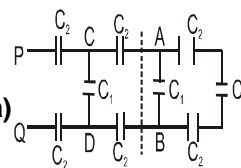
$$= \frac{1}{4\pi\epsilon_0} \left(\frac{4q}{5} \right)$$



11. [ACD](a)

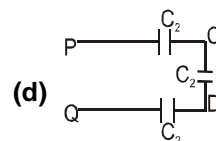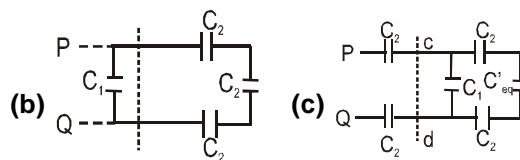

Let C'_{eq} be the equivalent capacity between points a and b. Obviously, from fig. (b)

$$C'_{eq} = C_1 + \frac{C_2}{3}$$

$$= 1 + \frac{3}{3} = 2 \sim F \quad \dots (i)$$

Similarly, the equivalent capacity C''_{eq} between points and d is

$$C''_{eq} = C_1 + \frac{C_2 C'_{eq}}{2C'_{eq} + C_2}$$

$$= 1 + \frac{3 \times 2}{4 + 3}$$

$$= 1 + \frac{6}{7} = \frac{13}{7} \mu F \quad \dots(ii)$$

If C is equivalent capacity between points P and Q, we note that $C_2 C_{eq} C_2$ are connected in series as shown in Fig (d)

Therefore,

$$\frac{1}{C_{eq}} = \frac{1}{C_2} + \frac{1}{C_2} + \frac{1}{C_{eq}}$$

or

$$C_{eq} = \frac{C_2 C_{eq}}{2C_{eq} + C_2}$$

$$= \frac{3 \times (13/7)}{2(13/7) + 3} = \frac{39}{47} \mu F$$

The total charge q on the arrangement is $q = C_{eq} \times V$

$$= \frac{39}{47} \times 410 \mu C = 340.2 \mu C \quad \dots(iv)$$

From fig (d) clearly capacitors $C_2 C_{eq}$ and C_2 are in series across 470 V.

12. [AC] Let cell delivers current i and i_1 is apart of current i that goes through R_3

So, by toop rule

$$E - iR_2 - i_1 R_3 - iR_1 = 0 \quad (\text{loop 1}) \dots(i)$$

$$i_1 R_3 (i - i_1) R_v = 0 \quad (\text{loop 2}) \dots(ii)$$

On solving for i_1 , Eq (ii) yields

$$i = \frac{R_3 - R_v}{R_v} \cdot i_1$$

Substituting this into Eq.(i), we get

$$E - \left(\frac{R_3 + R_v}{R_v} \right) R_2 i_1 - i_1 R_2 - \left(\frac{R_3 + R_v}{R_v} \right) R_1 i_1 = 0$$

$$\Rightarrow E = i_1 \left\{ \left(\frac{R_3 + R_v}{R_v} \right) R_2 - R_2 - \left(\frac{R_3 + R_v}{R_v} \right) R_1 \right\}$$

$$= i_1 \left\{ \frac{(R_3 + R_v)R_2 - R_v R_2 - (R_3 + R_v)R_1}{R_v} \right\}$$

$$\text{So, } i_1 = \frac{ER_v}{(R_3 + R_v)R_2 - R_v R_2 - (R_3 + R_v)R_1}$$

$$= \frac{3 \times 5 \times 10^3}{\left[(250 + 5 \times 10^3)300 - 5 \times 10^3 \right] \times 250 - (250 + 5 \times 10^3) \times 100}$$

and potential drop across resistance

$$R_3 = i_1 R_3 = 1.12V$$

Current in the absence of voltmeter is

$$i' = \frac{E}{R_1 + R_2 + R_3}$$

∴ True potential drop across

$$R_3 = i' R_3 = \frac{3 \times 250}{250 + 300 + 100} = 1.15V$$

So, fraction error is

$$\frac{1.15 - 1.12}{1.15} = 0.030$$

This is about 3%

13. [BD] The mass of a wire of length l , cross-sectional area A and density d is given by
 $m = Ald$


Since, A and d are the same for the two wires and since, their masses are in the ratio of 1 : 2, their lengths and hence, their resistance are in the ratio of 1 : 2, when the wires are connected in series, the same current I flows in each. Since, the heat H produced in time t is given by

$$H = I^2 R t \quad \text{or} \quad H \propto R$$

On the other hand, if the wires are connected in parallel, the potential difference V is the same across the two wires. Since, H is also given by

$$H = \frac{V^2 t}{R} \quad \text{or} \quad H \propto \frac{1}{R}$$

14. [ABC]

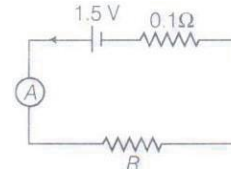

As ammeter shows 2A, an external resistance or R ohm is connected in the circuit.

$$I = \frac{V}{r + R}$$

$$2 \times (0.1 + R) = 1.5$$

$$0.2 + 2R = 1.5$$

$$2R = 1.3$$

$$R = \frac{1.3}{2} = 0.65 \Omega$$

Rate of chemical energy consumption

$$v = \frac{dQ}{dt} = vI = 1.5 \times 2 = 3W$$


Rate of energy dissipation in the cell

$$= I^2 r = 4 \times 0.1 = 0.4W$$


Rate of energy dissipation inside the resistor

$$= I^2 R = 4 \times 0.65 = 2.60W$$

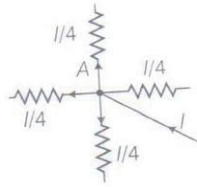
15. [AD] As, current enters through A and disubtes in infinite network. So, by symmetry current equally in 4 equal parts



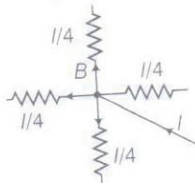
and current from circuit are directed towards B,




When we consider A and B as

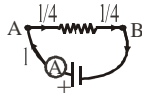

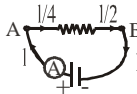So, currents in AB branch superimposes and $I_{AB} = \frac{I}{2}$



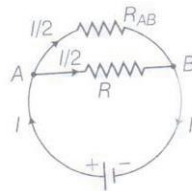and so we consider remaining circuit as R'_{AB}




Now, $V_{AB} = \frac{I}{2}R = \frac{I}{2}R_{eq} \Rightarrow R'_{eq} = \frac{R}{2}$

So, equivalent resistance is $\frac{R}{2}$.

Also, $V = IR_{eq}$

$$\Rightarrow I = \frac{V}{R_{eq}} = \frac{V}{R/2} = 2A$$

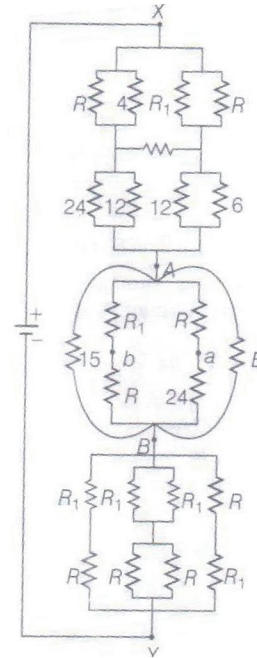16. [AC] Given circuit can be redrawn as,



If value of R_2 is changed, it has no effect on equivalent resistance of circuit.

\therefore Wheatstone bridge between X and Y is balanced.

$$\text{So, } \frac{\left(\frac{PR_1}{R+R_1}\right)}{\left(\frac{4R}{4+R}\right)} = \frac{\left(\frac{6 \times 12}{6+12}\right)}{\left(\frac{12 \times 24}{12+24}\right)}$$

On solving, we get $R_1 = \frac{4R}{4+2R} = \frac{2R}{2+R}$

17. [AD] Equivalent emf

$$\text{of three cells is } E_{eq} = \frac{\sum(E/r)}{\sum(1/r)} = 2V$$

Equivalent circuit is

Since, no current is drawn from cell,

$$V_{AB} = 2V \text{ and } V_{AB} = V_A - V_B = E_1 - i_1 r_1$$

$$\therefore i_1 = \frac{V_B - V_A + E_1}{r_1} = \frac{-2+3}{1} = 1A$$

$$i_2 = \frac{V_B - V_A + E_2}{r_2} = \frac{-2+3}{1} = 0$$

$$i_3 = \frac{V_B - V_A + E_3}{r_3} = \frac{-2+3}{1} = -1A$$

18. [ABC] Let us consider that ball is first touched to +ve plate, as a result, it acquires +ve charge and due to electric field from +ve to -ve plate, it accelerates and comes into contact with -ve plate. There it releases +ve accelerating from -ve to +ve plate and this process repeats.

19. [A] 252000J

20. [A] 201600 J

Obtain power dissipated as heat the remaining power is the sum of the mechanical power yielded by the motor and the chemical power stored in the battery.

21. [A] The emf of cell = potential drop of balance length = $xll_{(AC)}$

Here, $x = \frac{99\Omega}{99m} = \frac{1\Omega}{cm}$

I = current in potentiometer wire

$$= \frac{V_{AB}}{R_{AB}} = \frac{10V}{100\Omega} = \frac{1}{10} A$$


$$\therefore E = 1\Omega/cm \times \frac{1}{10} A \times 40cm = 4V$$

22. [A] When jockey is touched at point B, the circuit will be applying Kirchhoff's law.

$$-99i - i_1 + 10 = 0 \dots (i)$$


$$-99i - i_2 + 1 = 0 \dots (ii)$$
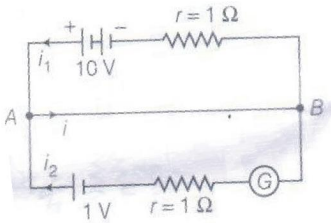
$$\text{and } i_1 + i_2 = i \dots (iii)$$



On solving these equations, we get i and potential

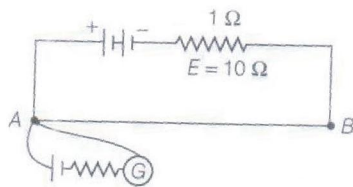23. [D] When jockey is touched at point A, then there are two separate loops.



24. [A] When jockey is touched at point A, then potential difference across the terminals of driver cell is given $V = E - Ir = 9.9 V$

$$25. [A] neA \hat{v}_d = i \Rightarrow \hat{v}_d = \frac{i}{neA}; t = \frac{l}{\hat{v}_d}$$

$$26. [A] neA \hat{v}_d = i \Rightarrow \hat{v}_d = \left(\frac{eE}{m}\right) \dagger \text{ and } \therefore \hat{v} = IR$$

$$\Rightarrow \frac{ne^2 AE \dagger}{m} = i \Rightarrow \left(u \sin gE = \frac{V}{L}\right)$$

$$\Rightarrow \dots = \frac{m}{ne^2 \dagger} \Rightarrow \dagger = \frac{m}{ne^2 l}$$

$$= \frac{9.1 \times 10^{-31}}{8 \times 10^{28} \times (1.6 \times 10^{-19})^2 \times (1.6 \times 10^{-8})} \approx 10^{-14}$$

27. [A]

$$\therefore V = iR \Rightarrow V = i \frac{\dots}{A} \times l = \frac{i \dots d t}{A}$$

28. [A] Wheatstone bridge is balanced.

$$\text{As, } \frac{P}{Q} = \frac{R}{S}$$

$$\Rightarrow \frac{40}{60} = \frac{60}{15} = \frac{4}{1}$$

$$\Rightarrow V_{AB} = V_{AD}$$

$$\text{So, } 40l_1 = 60l_2$$

$$l_1 = 1.5l_2$$

$$\text{Heat produced in AB} = I_1^2 R t = (1.5l_2)^2 \times 40 \times t = 90l_2^2 t$$

$$\text{Heat produced in BC} = I_1^2 R t = (1.5l_2)^2 \times 10 \times t = 22.5l_2^2 t$$

$$\text{Heat produced in AD} = I_2^2 R t = l_2^2 \times 60 \times t = 60l_2^2 t$$

$$\text{Heat produced in DC} = I_2^2 R t = l_2^2 \times 15 \times t = 15l_2^2 t$$

$$(i) \rightarrow (s), (ii) \rightarrow (r), (iii) \rightarrow (q), (iv) \rightarrow (p)$$


29. [B] (i) \rightarrow (q, r, s), (ii) \rightarrow (s), (iii) \rightarrow (p, q), (iv) \rightarrow (r)
All are Wheat stone bridge. Only S is balanced as

$$\frac{P}{Q} = \frac{R}{S}$$

To get direction of current, find V_B and V_D .

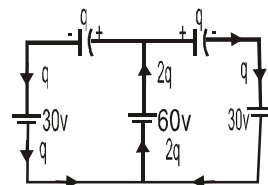[1.8] With switch S open the potential difference across t group of capacitors is zero. There is no charge on both of them.

With S closed, potential difference across both of them is 30 V. Charge on each of them is



$$q = (2\mu F)(30V) = 60\mu C$$

Polarity is as shown. The charge flow in various path has also been shown.

Energy supplied by 60 V cell = $60 \times 2q = 60 \times 120 \mu J$
Energy absorbed by each of 30 V cell = $30 \times q = 30 \times 60 \mu J$

$$\text{Energy stored in capacitor} = \frac{1}{2} CV^2 = \frac{1}{2} \times 2 \times 30^2 \mu J$$

$$\therefore \text{Heat dissipated} = 60 \times 120 - 2 \times 30 \times 60 - 2 \times 30^2$$

$$= 60[120 - 60 - 30]$$


$$= 60 \times 30 = 180\mu J = 1.8mJ$$

31. [0.6]

32. [1]

33. [1]

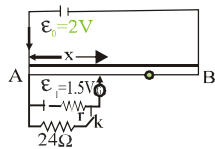34. [6] Let λ is resistance per unit length of wire AB. When k is opened



$$I(x_1) = E_1 \quad \dots(\text{i})$$

k is closed $I(x_2) = E_1 - ir \quad \dots(\text{ii})$

$$i = \frac{E_1}{R + r} \quad \dots(\text{iii})$$

$$\Rightarrow r = \left(\frac{x_1}{x_2} - 1 \right) R = \left(\frac{0.75}{0.60} - 1 \right) 24; r = 6\Omega$$