

ANSWERS AND SOLUTIONS

Ques.	1	2	3	4	5	6	7	8	9
Ans.	B	A	D	B	C	A	A,B	A,BC	A,D
Ques.	10	11	12	13	14	15	16	17	18
Ans.	A,B	A,C,D	B,C,D	2	6	6	3	4	1


1. Terminal velocity is attained when magnetic force is equal to $mg \sin \theta$

$$F_m = mg \sin \theta$$

Or $i l B = mg \sin \theta$ Or $\left(\frac{e}{R}\right) I B = mg \sin \theta \therefore$

Or $\frac{(B v_T I)}{R} I B = mg \sin \theta$

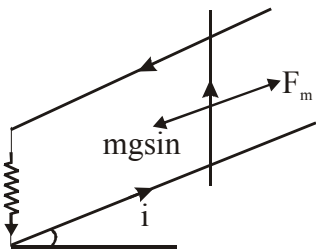
$$\therefore v_T = \frac{mgR \sin \theta}{B^2 I^2}$$



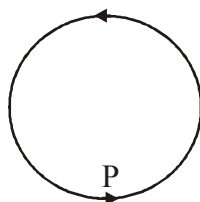2. $E I = \frac{d\phi}{dt} \therefore E(2\pi R) = (\pi R^2) \frac{dB}{dt} \therefore$

$$E = \frac{R}{2} \frac{dB}{dt} \quad q = \frac{qE}{m} = \frac{eR}{2m} \frac{dB}{dt}$$

At 'P' induced electric lines towards right, force on electron will be towards left



3. L : R

$$0.6 = \frac{R}{\sqrt{R_1^2 + X_L^2}} \quad \dots(1)$$

$$0.5 = \frac{R_2}{\sqrt{R_2^2 + X_C^2}} \quad \dots(2)$$

$$I = \frac{R_1 + R_2}{\sqrt{(R_1 + R_2)^2 + (X_L + X_C)^2}} \quad \dots(3)$$

Solving these three equations we get,

$$\frac{R_1}{R_2} = \frac{3\sqrt{3}}{4}$$

4. Frequency $f \propto \sqrt{mg}$ or $f \propto \sqrt{g}$

In water $f_m = 0.8 f_{air}$

$$\therefore \frac{g'}{g} = (0.8)^2 = 0.64 \text{ Or } 1 - \frac{\rho_w}{\rho_m} = 0.64$$

$$\text{Or } \frac{\rho_w}{\rho_m} = 0.36$$

$$\text{In liquid } \frac{g'}{g} = (0.6)^2 = 0.36 \therefore 1 - \frac{\rho_L}{\rho_m} = 0.36$$

$$\text{Or } \frac{\rho_L}{\rho_m} = 0.64$$

From Eqs. (1) and (2)

$$\frac{\rho_L}{\rho_w} = \frac{0.64}{0.36} \therefore \rho_L = 1.77 \text{ Here, } \rho_w = \text{relative}$$

density of water = 1

ρ_m = relative density of mass

And ρ_L = relative density of liquid.

5 We consider a small portion Dl of the loop.

For equilibrium,

$$F = 2T \frac{\sin \theta}{2} = 2T \frac{\theta}{2} = T\theta$$

or $ID/B = Tq$

$$6 \quad R = \frac{mv}{qB} = \frac{P}{qB}$$

But kinetic energy $T = \frac{P^2}{2m} \quad P = \sqrt{2mT}$

$$\therefore R = \frac{\sqrt{2mT}}{qB}$$

$$\therefore R' = \frac{\sqrt{2m(2T)}}{q(3B)}$$

$$R' = \frac{\sqrt{2}}{3} R = \sqrt{\frac{2}{9}} R$$

Hence, option (C) is correct.

$$7. \quad X_C = \frac{1}{2\pi fC} = \frac{1}{(2\pi)(50/\pi)(0.02 \times 10^{-3})} = 500\Omega$$

$$X_L = 2\pi fL = (2\pi)(50/\pi)(1) = 100\Omega$$

$$Z = \sqrt{R^2 + (X_C - X_L)^2} = 500\Omega$$

$$i_{\text{rms}} = \frac{E_{\text{rms}}}{Z} = 0.1A \quad (V_C)_{\text{rms}} = i_{\text{rms}} X_C = 50V$$

$$8. \quad |e| = \left| \frac{d\phi}{dt} \right| = 4t \therefore i = \frac{|e|}{R} = 0.4t$$

At $t = 2s$, $i = 0.8A$

$i-t$ graph is straight line passing through origin.

$$\Delta q = \int_0^2 i dt = \int_0^2 0.4t = 0.8C$$

9. This is a L-C circuit. Therefore,

$q = q_0 \cos \omega t$

And $V = V_0 \cos \omega t$

$$\text{Where } \omega = \frac{1}{\sqrt{LC}}$$

$$\text{Or } T = 2\pi / \sqrt{LC}$$

$$i = \frac{dq}{dt} = -q_0 \omega \sin(\omega t)$$

(a) maximum current in the circuit is

$$i_{\text{max}} = q_0 \omega = (CV_0) \frac{1}{\sqrt{LC}} = V_0 \sqrt{\frac{C}{L}}$$

(b) potential across capacitor becomes zero after time $t = \frac{T}{4} = \frac{\pi}{2} \sqrt{LC}$

$$\text{ter time } t = \frac{T}{4} = \frac{\pi}{2} \sqrt{LC}$$

(c) at time $t = \frac{\pi}{2} \sqrt{LC}$ or $T/4$ energy stored in

the capacitor is zero. Thus, the energy $\frac{1}{2} CV_0^2$

will be stored in the inductor.


(d) the maximum energy stored in the inductor

will be $\frac{1}{2} CV_0^2$.

$$10. \quad \vec{\tau} = \vec{P} \times \vec{E} \quad U = -\vec{P} \cdot \vec{E}$$

$$U_{\text{max}} = PE$$

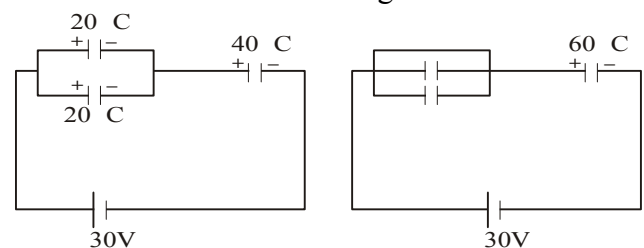11. The charges stored in different capacitors before and after closing the switch S are



$$\frac{40 \times \cancel{Z}}{\cancel{\theta}_3} = \frac{4}{\cancel{\theta}} (3\theta)^{10}$$

The amount of charge flown through the battery is $q = 20\mu C$

\therefore Energy S supplied by the battery is

$$U = qV = (20 \times 10^{-6})(30)J$$

$$U = 0.6 \text{ mJ}$$

Energy stored in all the capacitors before closing the switch S is

$$U_i = \frac{1}{2} C_{\text{net}} V^2 = \frac{1}{2} \left(\frac{4}{3} \times 10^{-6} \right) (30)^2$$

$$= 0.6 \text{ mJ}$$

And after closing the switch

$$U_f = \frac{1}{2} C_{\text{net}} V^2 = \frac{1}{2} (2 \times 10^{-6}) (30)^2 = 0.9 \text{ mJ}$$

$$\therefore \text{Heat generated } H = U - (U_f - U_i) = 0.3 \text{ J}$$

And charge flown through the switch is $60 \mu\text{C}$

$$12. \quad \tau_{C_1} = \tau_{C_2} = 2CR = \tau_c \quad (\text{say})$$

$$q_1 = (EC)(1 - e^{-t/\tau_c})$$

$$\text{And } q_2 = (2EC)(1 - e^{-t/\tau_c})$$

$$\frac{q_1}{q_2} = \frac{1}{2} \quad (\text{at any time})$$

\therefore The ration of steady state charge is also 1 : 2

$$\left(\frac{dq_1}{dt} \right) = \frac{EC}{\tau_c} e^{-t/\tau_c}$$

$$\text{And } \left(\frac{dq_2}{dt} \right) = \frac{2EC}{\tau_c} e^{-t/\tau_c}$$

$$\therefore \left(\frac{dq_1}{dt} \right) \neq \left(\frac{dq_2}{dt} \right)$$

\therefore Option (a) is wrong.

$$13. \quad \frac{di}{dt} = \omega^2 q$$

$$= \frac{q}{LC} = \frac{3.0 \times 10^{-5}}{0.6 \times 25 \times 10^{-6}} = 2 \text{ A / s}$$

$$14. \quad i_{\text{rms}}^2 = \frac{\int i dt}{\int dt}$$

$$= \frac{\int_2^4 (4t) dt}{\int_2^4 dt} = \frac{4 \int_2^4 t dt}{2} = 2 \left[\frac{t^2}{2} \right]_2^4$$

$$= 12 \text{ A}^2$$

$$i_{\text{rms}} = 2\sqrt{3} \text{ A}$$

$$15. \quad q = (2\mu\text{F})(60\text{V}) = 12 \mu\text{C},$$

$$q_0 = (2\mu\text{F})(12\text{V}) = 24\mu\text{C}$$

$$\omega = \frac{2}{\sqrt{LC}} = \frac{1}{\sqrt{0.6 \times 10^{-3} \times 2 \times 10^{-6}}}$$

$$= 2.9 \times 10^4 \text{ rad/s}$$

$$i = \omega \sqrt{q_0^2 - q^2}$$

$$= (2.9 \times 10^4)(10^{-6}) \sqrt{(24)^2 - (12)^2} = 0.6 \text{ A}$$

16 Before connecting with wire, the total electrical energy is

$$U_i = \frac{q^2}{8\pi\epsilon_0 a}$$

After connection with wire, all charges are transferred on outer sphere.

$$\therefore U_f = \frac{q^2}{8\pi\epsilon_0 b}$$

$$\omega = 3 \text{ rad/s.}$$

17 If radii of spherical capacitor are 'a' and 'b' and air is filled between them, then

$$C = \frac{4\pi\epsilon_0 ab}{b-a}$$

$$\text{Given, } b - a = x = 1 \text{ mm} = 10^{-3} \text{ m}$$

$$a = b - x, C = 10^{-6} \text{ F}$$

$$\therefore 10^{-6} = \frac{(b-x)b}{9 \times 10^9 \times 10^{-3}}$$

$$\text{or } b(b-x) = 9 \quad (\because x \ll b)$$

$$\text{or } b^2 = 9$$

$$\therefore b = 3$$

$$18. \quad \lambda_\alpha - \lambda_m = 3(\lambda_\alpha - \lambda_m)$$

$$\therefore \frac{12375}{10.2(z-1)^2} - \frac{12375}{20 \times 10^3} = 3 \left[\frac{12375}{10.2(z-1)^2} - \frac{12375}{10 \times 10^3} \right]$$

Solving we get $z = 29$